

Semiconductor

p-type -

Holes

$$I_n \gg I_e$$

Holes are Majority Carrier

★ P & n p n



Holes Junction Electrons

Depletion

Layer

V_B = Barrier potential

$$V_B = 0.7 \text{ V (Si)}$$

n-type -

electron

$$I_n \ll I_e$$

electrons are Majority Carriers.

★ Rectifier

— AC Voltage Converted to DC Voltage.

● output Contains Some AC Component.

— Remained AC Component is Ripples.

— Ripples is Removed by using filter Circuit.

— Output of filter is almost pure DC current.


— Voltage Regulator Restricts 'V' to desired Values.

★ Rectification \rightarrow Conversion of AC Voltage to DC Voltage.

★ Rectifier \rightarrow Device converting AC Voltage to DC Voltage.

① Half Wave Rectifier

P-n Junction diode

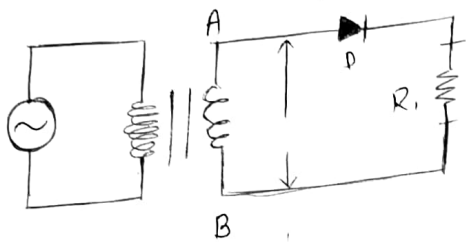

Input \rightarrow



output \rightarrow




Discontinuous

Unidirectional

In first half D conducts and in second half D doesn't conduct. As Diode doesn't conduct in Reversed Bias mode.

② Full Wave Rectifier

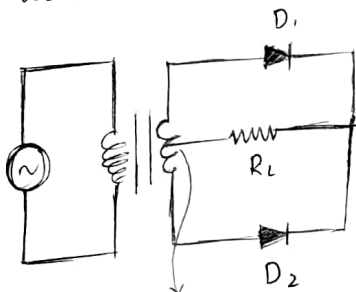

- For the first half D_1 will conduct D_2 doesn't
- For second half D_2 conducts and D_1 doesn't.

- Centre tapped Secondary Coil

- acts as Common Cathode

Input \rightarrow




$D_1 \rightarrow$



$D_2 \rightarrow$



Output \rightarrow

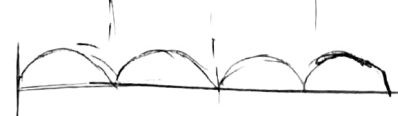

Continuous and Unidirectional.

Advantages of Full Wave Rectifier.

- 1.) Rectification takes place in both the cycles of the AC Input.
- 2.) Efficiency of a full Wave Rectifier is higher than half wave rect.
- 3.) The ripple in a full wave Rectifier is less than that in a half wave Rectifier.

★ Ripple Factor.


— The Ratio of Root mean (rms) Value of the AC Component to the Value of the DC Component in the Rectifier output.

$$\text{Ripple factor} = \frac{\text{r.m.s Value of A.C Component}}{\text{r.m.s Value of D.C Component}}$$

★ Filter Circuit

— Removes the Remaining AC Component from the output of Rectifier.

★ A Capacitor filter

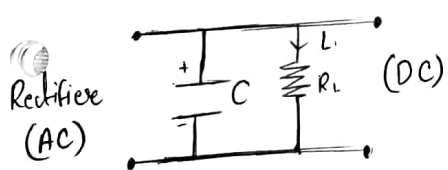

- Capacitor gets charged at the peak Value.
- And Whenever the Voltage drops the Capacitor provides its Stored Charge.
- Due to which the AC Component Reduces.

★ Zener Diode.

It is a Special type of Diode which works in Reversed biased Mode.



★ Zener Breakdown / Junction Breakdown.

- If Voltage more than Barrier potential Breakdown occurs and Current flows.
- Zener diode is a Special P-n Junction diode which is

Heavily Doped.


- Always Connected Reversed Biased.

- Always in parallel with load.


- Initially Very Small is flowing but if we Increase the Input Voltage the depletion layer breakdown occurs and No. holes and Electrons Increase.

★ Zener diode Characteristics

- After Breakdown Current Flow Increases

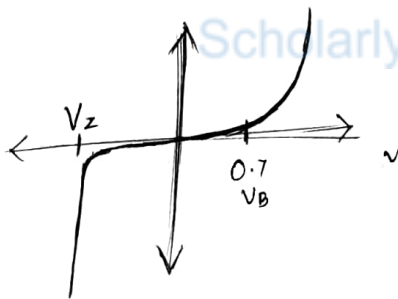

★ Zener Diode as Voltage Regulator.

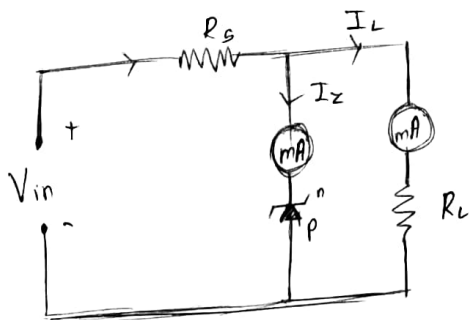

- Output Voltage is Always Constant

- Whenever more Current flows Zener diode absorbs excess Current.

★ Applications of Zener Diode.

- ① Used when Constant Voltage Required.
- ② It has many applications like:- Voltage Regulator, Fixed refn. Voltage provider etc.


★ Photo Diode

Special p-n junction diode which Converts light Energy to Electrical Energy.



- generates Current when Exposed to light.
- Also Called photodetector or a photo sensor.
- It operates in Reverse Bias mode.



★ Working of Photo diode.

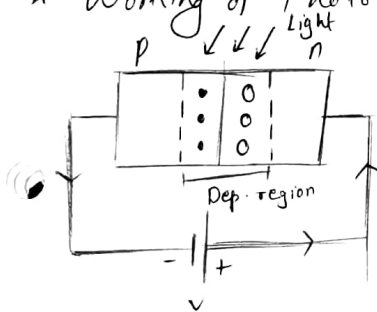

- light falls on the depletion Region.
- Then it Breaks the Bond.
- No. Holes & electrons are generated and Current Flows.

Dark Current - Very Small Currents flows when No light is there.

★ I - V Characteristics of photo diode.

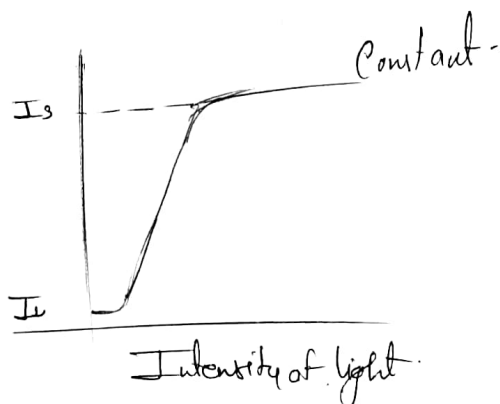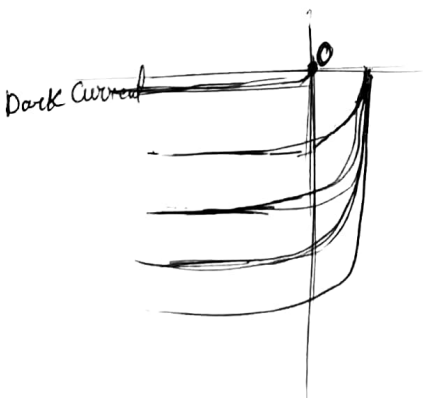


★ Applications of Photo diode

- Counters and Switches.
- Burglar alarm
- Fiber optics
- and many more.

★ Solar Cell / photo Voltaic Cell


- Converts Solar Energy into Electrical energy using Solar Cells.

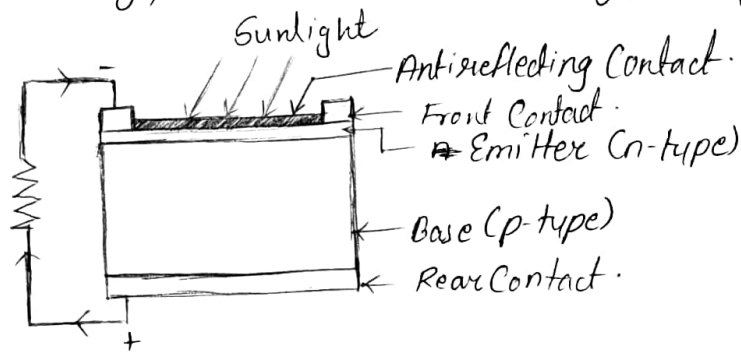- n-type is kept small so that light comes inside quickly



- Antireflecting Coating absorbs only the Visible light and radiation like I.R are Reflected so that the diode doesn't heat up.
- As Sunlight Enters it Breaks bond and Create electro-hole pair
- holes Come down and electrons go up and a potential difference is Created.
- As load Resistance gets Connected the Current Starts flowing.

★ V-I Characteristics of Solar Cell


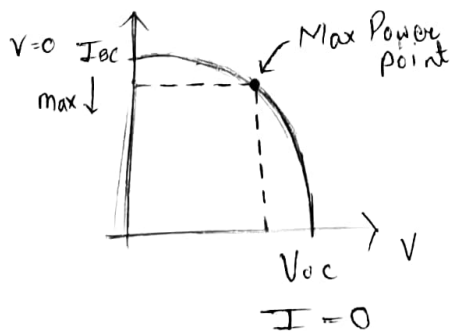


* Uses of Solar Cell

- ① Used for Charging batteries during day
- ② Calculators, Satellite, Traffic Signal, lux meter and etc

* Light Emitting Diode / LED

— Always Connected in Forward bias.

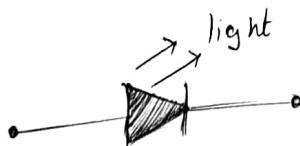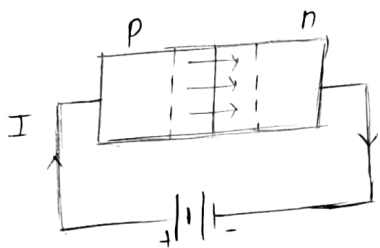

— When electron-hole pairs will start merging they will emit light

* I-V Characteristics of LED.



* Advantages of LED

- ① Energy efficient
- ② Long lasting.
- ③ Rugged.
- ④ No warm up period.
- ⑤ Excellent Color
- ⑥ Environment Friendly
- ⑦ Controllable



* Disadvantages of LED.

- ① Hazardous blue light.
- ② Temperature dependence
- ③ Voltage Sensitive.
- ④ high Initial Cost.

★ Bipolar Junction Transistor (BJT)

Junction transistor is a Semiconductor device having two junctions and three terminals. The current in a transistor is carried by both the electrons and the holes, Hence it is called bipolar junction transistor.


① n-p-n transistor.

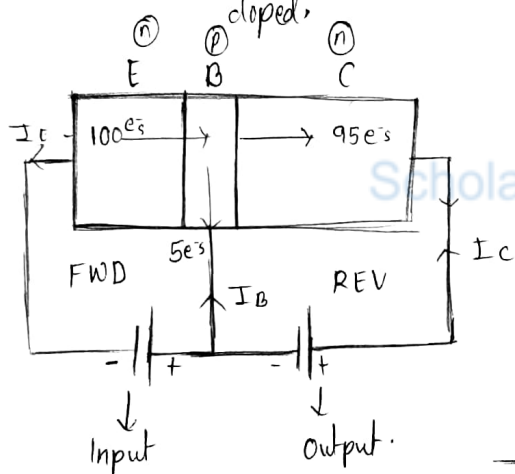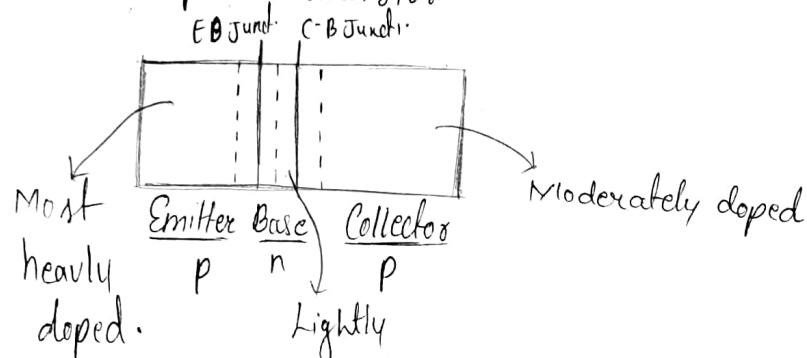

Common Base Configuration.


$$I_E = I_B + I_C$$

V: Small.

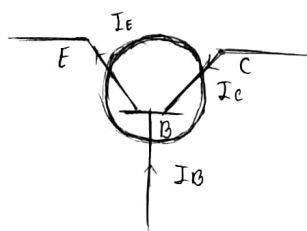


For p-n-p the direction will be opposite.


★ Common Emitter (CE) Config.

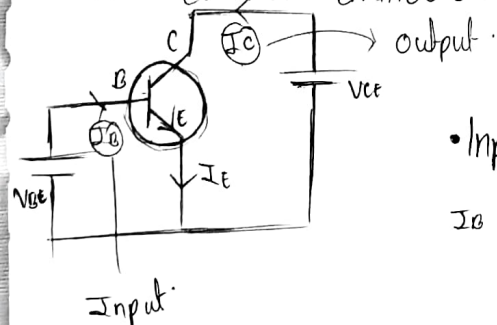

• Input Characteristic.

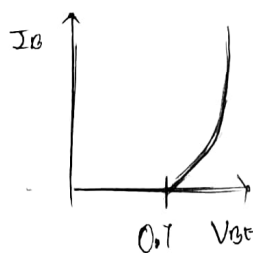

• Output Characteristics

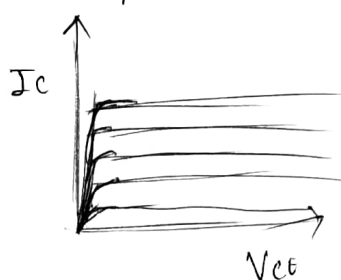

$$\beta = \frac{I_C}{I_B} \quad \alpha = \frac{I_C}{I_E}$$

Logic Gates

Same as Maths One (1 = True, 0 = False)



Not Gate.



OR Gate



AND Gate.



NAND Gate.

(Take it like Negation of AND)



NOR Gate

(Negation of OR)

NAND } Universal Gates
NOR }



Exclusive OR/X-OR Gate.

A	B	\bar{A}	\bar{B}	$\bar{A} \cdot B + A \cdot \bar{B}$
0	0	1	1	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0